
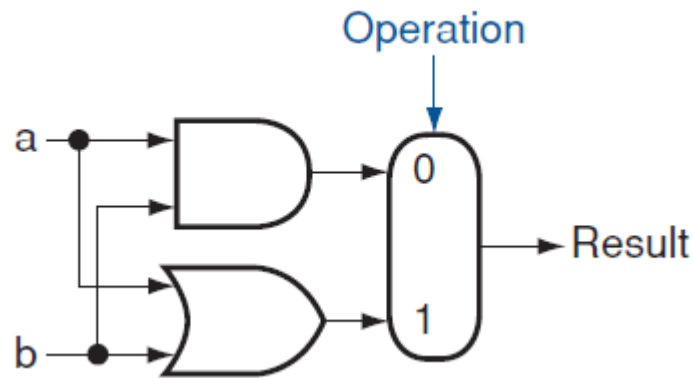


- The ALU is the brawn of the computer
- Performs integer arithmetic operations
  - Addition and subtraction
  - Multiplication and division
- Performs logical operations
  - AND, OR, XOR
- Acts on commands from control unit

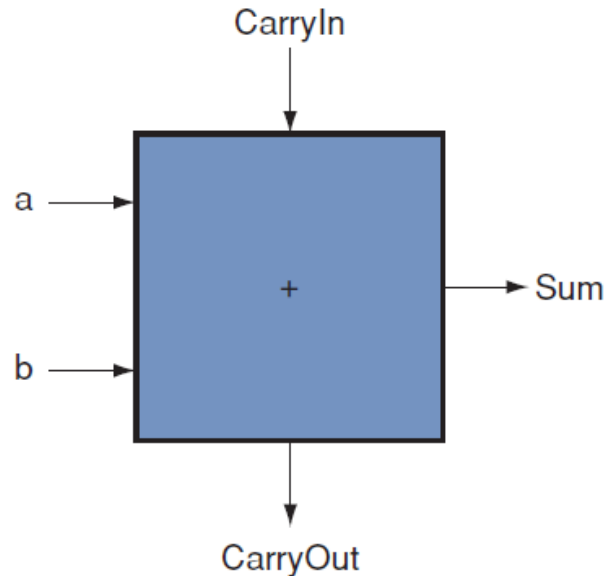- Multiple 1-bit ALUs can be used to build a 32-bit ALU
- This is called a bit sliced design
- The AND and OR operations map directly to gates




- From module 3 we know how to build a full adder



- The single bit inputs (a and b) together with the Carryin are added to produce the Sum and Carryout


- Truth table and possible circuit to generate CarryOut

Inputs		
a	b	CarryIn
0	1	1
1	0	1
1	1	0
1	1	1

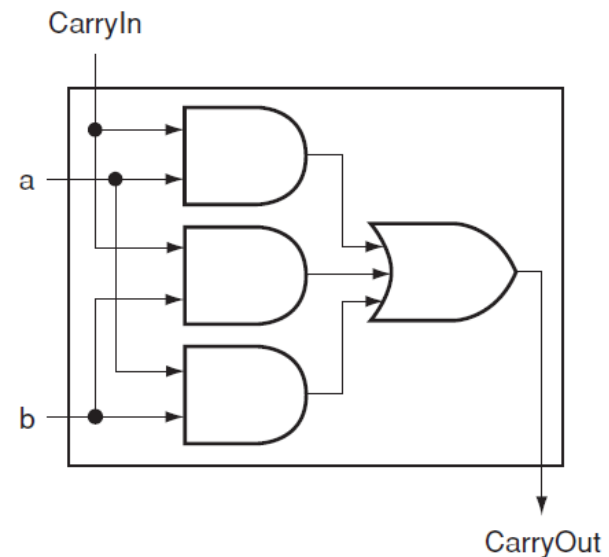

$$\begin{aligned}\text{CarryOut} &= (a \cdot \text{CarryIn}) + (a \cdot b) + (b \cdot \text{CarryIn}) \\ &= (a \cdot b) + (a + b) \cdot \text{CarryIn}\end{aligned}$$

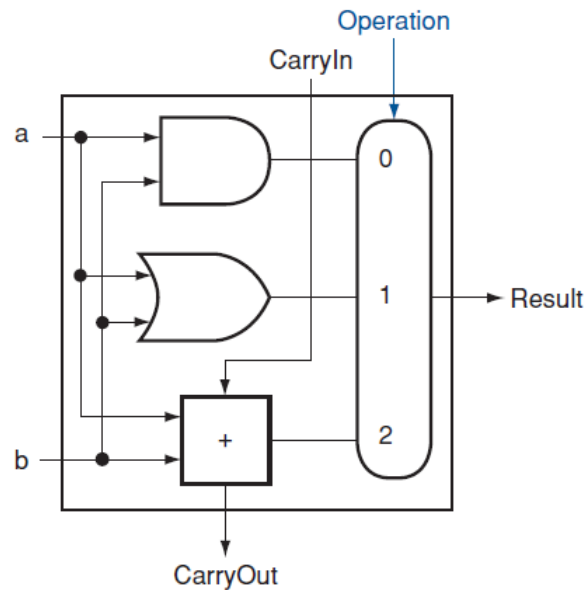- 1-Bit ALU containing AND gate, OR gate and Full adder



- Full 32-Bit ALU can be built up from multiple copies


Subtraction can be included by noting that:

$$a + \bar{b} + 1 = a + (\bar{b} + 1) = a + (-b) = a - b$$


$\bar{b} + 1$  is the negative of  $b$

Subtract  $b$  from  $a$  by adding the negative of  $b$  to  $a$

Uses two's complement of  $b$

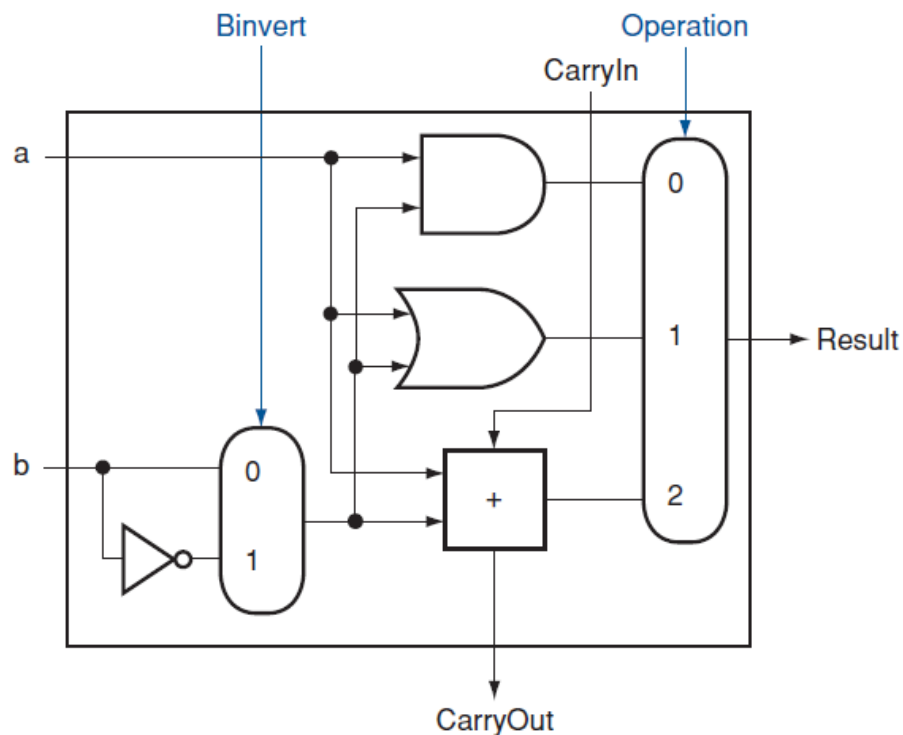

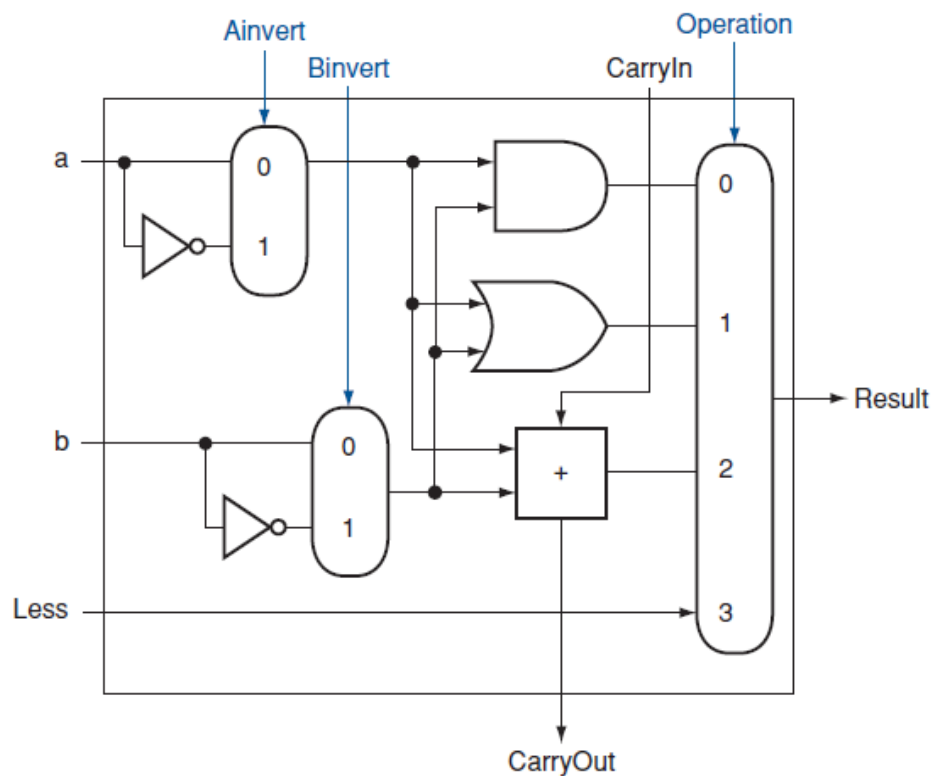1-Bit ALU that subtracts, adds and performs AND and OR



Ainvert allows the computation of  $(b - a)$  and other functions