


State register holds
state number

State alone is sufficient to determine output control signals

Output	Current states	Op
PCWrite	state0 + state9	
PCWriteCond	state8	
IorD	state3 + state5	
MemRead	state0 + state3	
MemWrite	state5	
IRWrite	state0	
MemtoReg	state4	
PCSource1	state9	
PCSource0	state8	
ALUOp1	state6	
ALUOp0	state8	
ALUSrcB1	state1 + state2	
ALUSrcB0	state0 + state1	
ALUSrcA	state2 + state6 + state8	
RegWrite	state4 + state7	
RegDst	state7	

State alone determines output control signals

Output	Current states
PCWrite	state0 + state9
PCWriteCond	state8
IorD	state3 + state5
MemRead	state0 + state3
MemWrite	state5
IRWrite	state0
MemtoReg	state4
PCSource1	state9
PCSource0	state8
ALUOp1	state6
ALUOp0	state8
ALUSrcB1	state1 + state2
ALUSrcB0	state0 + state1
ALUSrcA	state2 + state6 + state8
RegWrite	state4 + state7
RegDst	state7

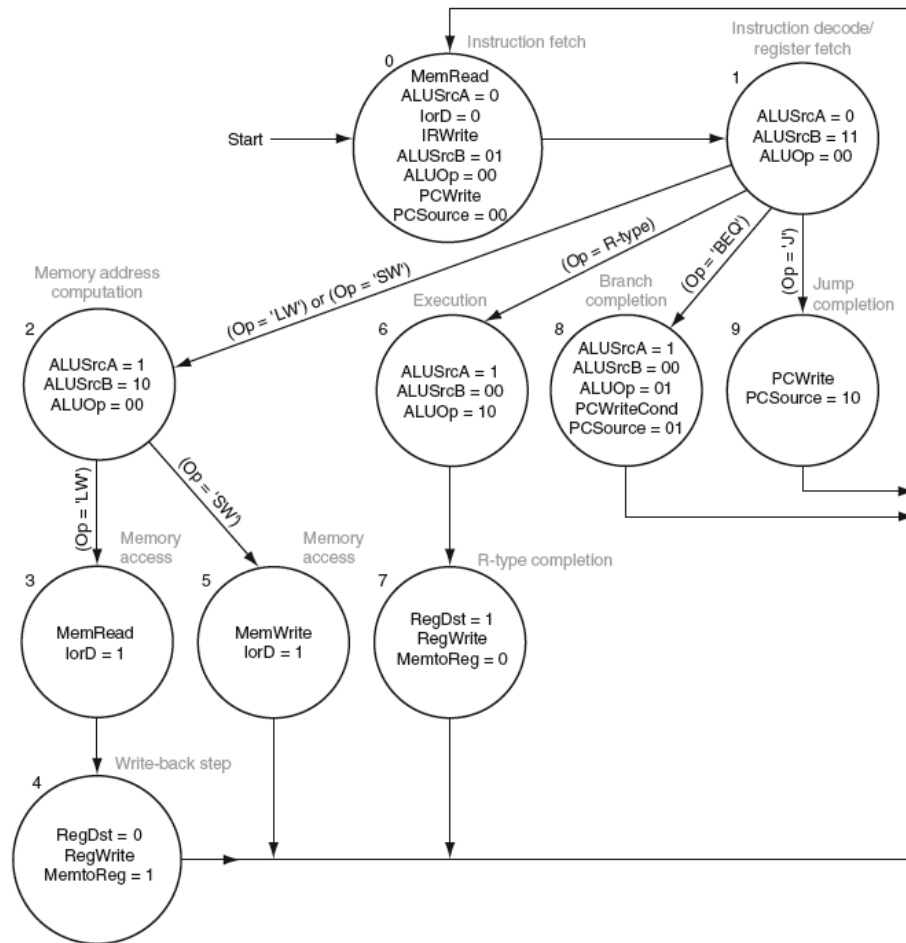

Opcode as well as state are needed to determine next state


Output	Current states	Op
NextState0	state4 + state5 + state7 + state8 + state9	
NextState1	state0	
NextState2	state1	(Op = 'lw') + (Op = 'sw')
NextState3	state2	(Op = 'lw')
NextState4	state3	
NextState5	state2	(Op = 'sw')
NextState6	state1	(Op = 'R-type')
NextState7	state6	
NextState8	state1	(Op = 'beq')
NextState9	state1	(Op = 'jmp')

Four bits are needed for state number (since there are 10 states)

Output	Current states	Op
NextState0	state4 + state5 + state7 + state8 + state9	
NextState1	state0	
NextState2	state1	(Op = 'lw') + (Op = 'sw')
NextState3	state2	(Op = 'lw')
NextState4	state3	
NextState5	state2	(Op = 'sw')
NextState6	state1	(Op = 'R-type')
NextState7	state6	
NextState8	state1	(Op = 'beq')
NextState9	state1	(Op = 'j')

Opcode as well as state are needed to determine next state

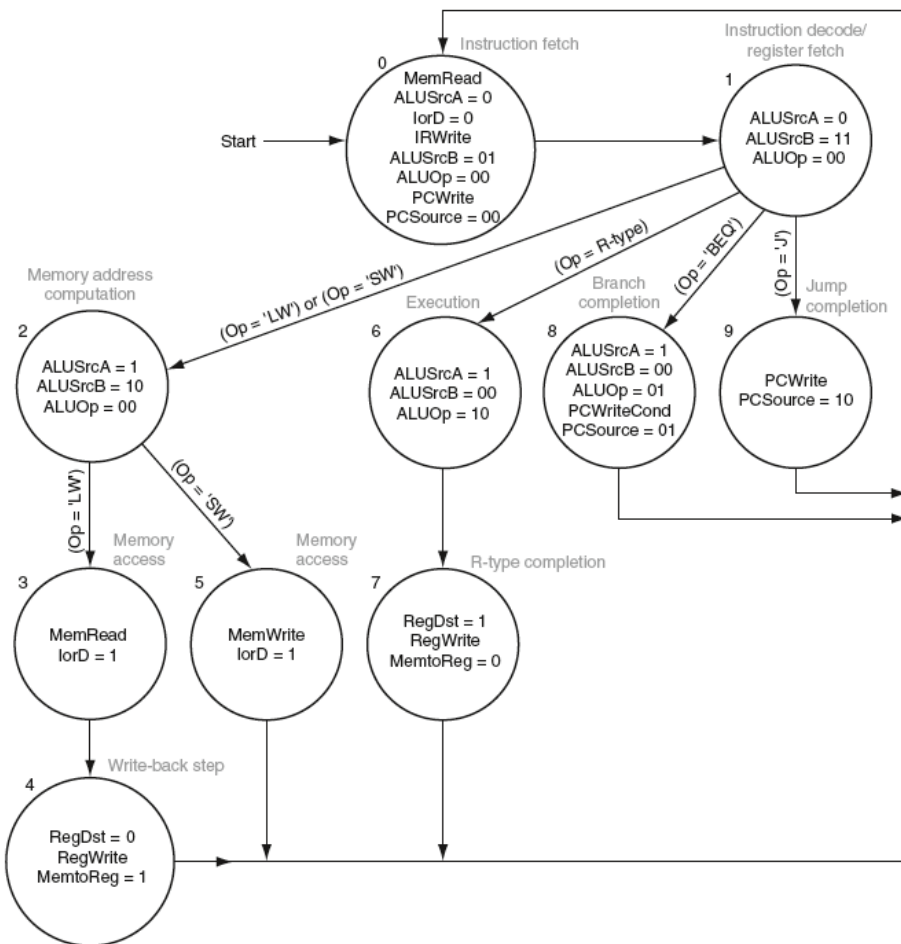Four bits are needed for state number (since there are 10 states)



Outputs	Input values (S[3-0])									
	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001
PCWrite	1	0	0	0	0	0	0	0	0	1
PCWriteCond	0	0	0	0	0	0	0	0	1	0
IorD	0	0	0	1	0	1	0	0	0	0
MemRead	1	0	0	1	0	0	0	0	0	0
MemWrite	0	0	0	0	0	1	0	0	0	0
IRWrite	1	0	0	0	0	0	0	0	0	0
MemtoReg	0	0	0	0	1	0	0	0	0	0
PCSource1	0	0	0	0	0	0	0	0	0	1
PCSource0	0	0	0	0	0	0	0	0	1	0
ALUOp1	0	0	0	0	0	0	1	0	0	0
ALUOp0	0	0	0	0	0	0	0	0	1	0
ALUSrcB1	0	1	1	0	0	0	0	0	0	0
ALUSrcB0	1	1	0	0	0	0	0	0	0	0
ALUSrcA	0	0	1	0	0	0	1	0	1	0
RegWrite	0	0	0	0	1	0	0	1	0	0
RegDst	0	0	0	0	0	0	0	1	0	0

Truth table gives the 16 control signals as function of 4-bit state

The 16 control signals could be read from a lookup table in ROM

Lower 4 bits of the address	Bits 19–4 of the word
0000	10010100000001000
0001	0000000000011000
0010	0000000000010100
0011	0011000000000000
0100	0000001000000010
0101	0010100000000000
0110	0000000001000100
0111	0000000000000011
1000	0100000010100100
1001	1000000100000000

Use state number as index or address in ROM LUT (lookup table)

Use state number (as row) and opcode (as column) to get next state number from second ROM LUT

	Op [5-0]					
Current state S[3-0]	000000 (R-format)	000010 (jmp)	000100 (beq)	100011 (lw)	101011 (sw)	Any other value
0000	0001	0001	0001	0001	0001	0001
0001	0110	1001	1000	0010	0010	Illegal
0010	XXXX	XXXX	XXXX	0011	0101	Illegal
0011	0100	0100	0100	0100	0100	Illegal
0100	0000	0000	0000	0000	0000	Illegal
0101	0000	0000	0000	0000	0000	Illegal
0110	0111	0111	0111	0111	0111	Illegal
0111	0000	0000	0000	0000	0000	Illegal
1000	0000	0000	0000	0000	0000	Illegal
1001	0000	0000	0000	0000	0000	Illegal

Undefined state/opcode combinations are “illegal”

- State number alone is sufficient to determine the 16 control bits
- The 4-bit state number and 6-bit opcode form a 10-bit address
- 10-bit address determines control bits as well as next state
- Instruction execution corresponds to a sequence of states
- Control bits output in each state direct datapath actions
- Each state is one step in the execution and takes 1 clock cycle
- Other control unit implementations will be described next.

Lookup Tables can consume large amounts of storage

Using a full 10-bit address (opcode + state) means 1024 entries

Each entry contains 16 control bits and 4 next state bits

Total size = $1024 * 20$ bits (expensive in earlier days of computing)


One way to reduce the required storage is to use a PLA


“PLA” means programmable logic array

Each PLA output is a logical sum of one or more minterms

Minterm (or product term) is a logical AND of two or more inputs

 A minterm corresponds to a single row in a truth table



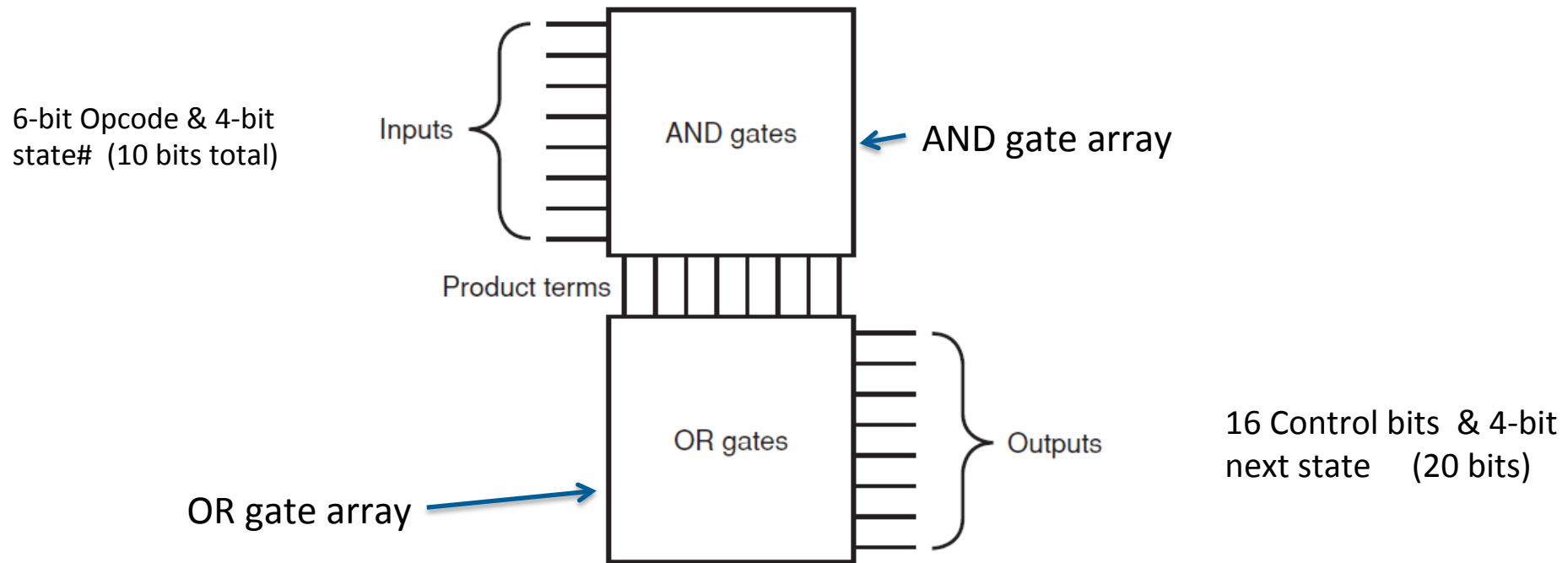


- AND array generates products of inputs or inverted inputs
- OR array generates logical sums of product terms

Programmable Logic Array

One vertical line for
each of the 17
minterms

 
Size proportional to
 $(\text{\#inputs} + \text{\#outputs}) * \text{\#product_terms}$



Horizontal output
lines correspond to
control lines and
next state bits

The 10 Inputs are
opcode and current
state

 Size proportional to
 $(10 + 20) * 17 = 510$



The 20 outputs are
control signals and
next state

Opcode bits and current state# and fed in for each cycle

The PLA outputs the resulting control signals and next state#

Control signals are output for each instruction step or subcycle

The sequence of state numbers identify the steps or transitions

This PLA supports our MIPS core instruction subset

Each vertical line in the previous PLA is a minterm

The leftmost 10 depend only on the state

The remaining 7 depend on the state and opcode

The top half of the figure is the AND plane that computes minterms

Dots in top half indicate which inputs are fed into AND gate

The bottom half is the OR plane that sums the minterms

Dots in lower half indicate which minterms are fed into OR gate


These 10 minterms depend only on state#

These 7 minterms depend on opcode as well as state#

Blue dots identify AND gate inputs

Black dots identify OR gate inputs

OR gates produce the sum of products

 

Previous PLA can be replaced by two smaller PLAs (PLA1 & PLA2)

PLA1

produces 10 minterms from 4 inputs (state)

outputs the 16 control signal bits

$$\text{Size} = (4 + 16) * 10 = 200$$

PLA2

produces 7 minterms from 10 inputs (opcode & state)

outputs 4-bit next state number

$$\text{Size} = (10 + 4) * 7 = 98$$

Together the two consume less space than the single larger PLA


- Most of the control logic is needed just for the next state number
- Our core MIPS system only has 10 states
- More realistic systems would have many more states
- Often the next state is just the previous state + 1
- The start state always comes after the final state in each instruction
- The start state begins the next instruction

State1 always comes
after state0


State4 always comes
after state3

State7 always comes
after state 6

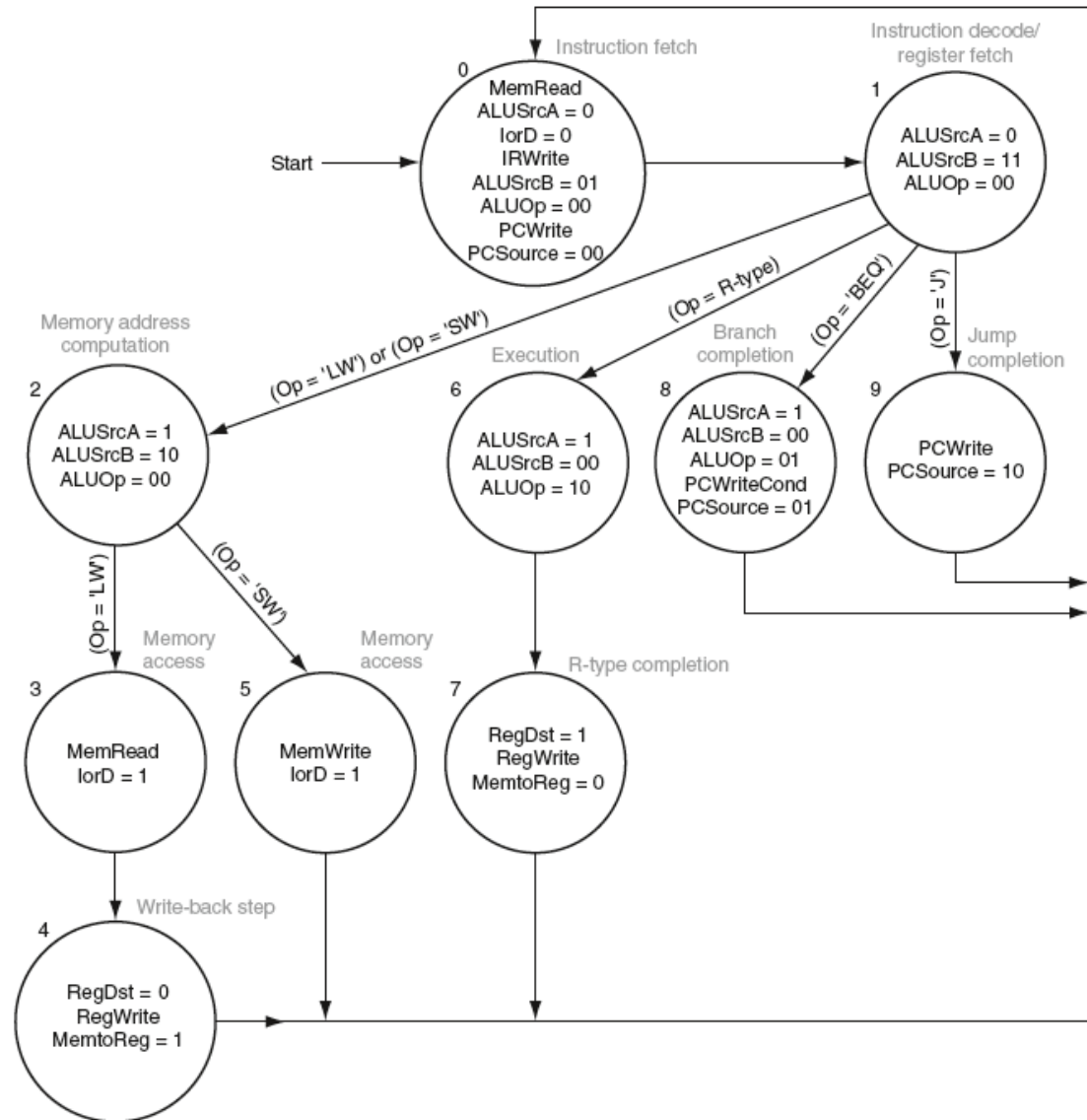State0 always comes
after states 4, 5, 7, 8
and 9



2-way choice from state2

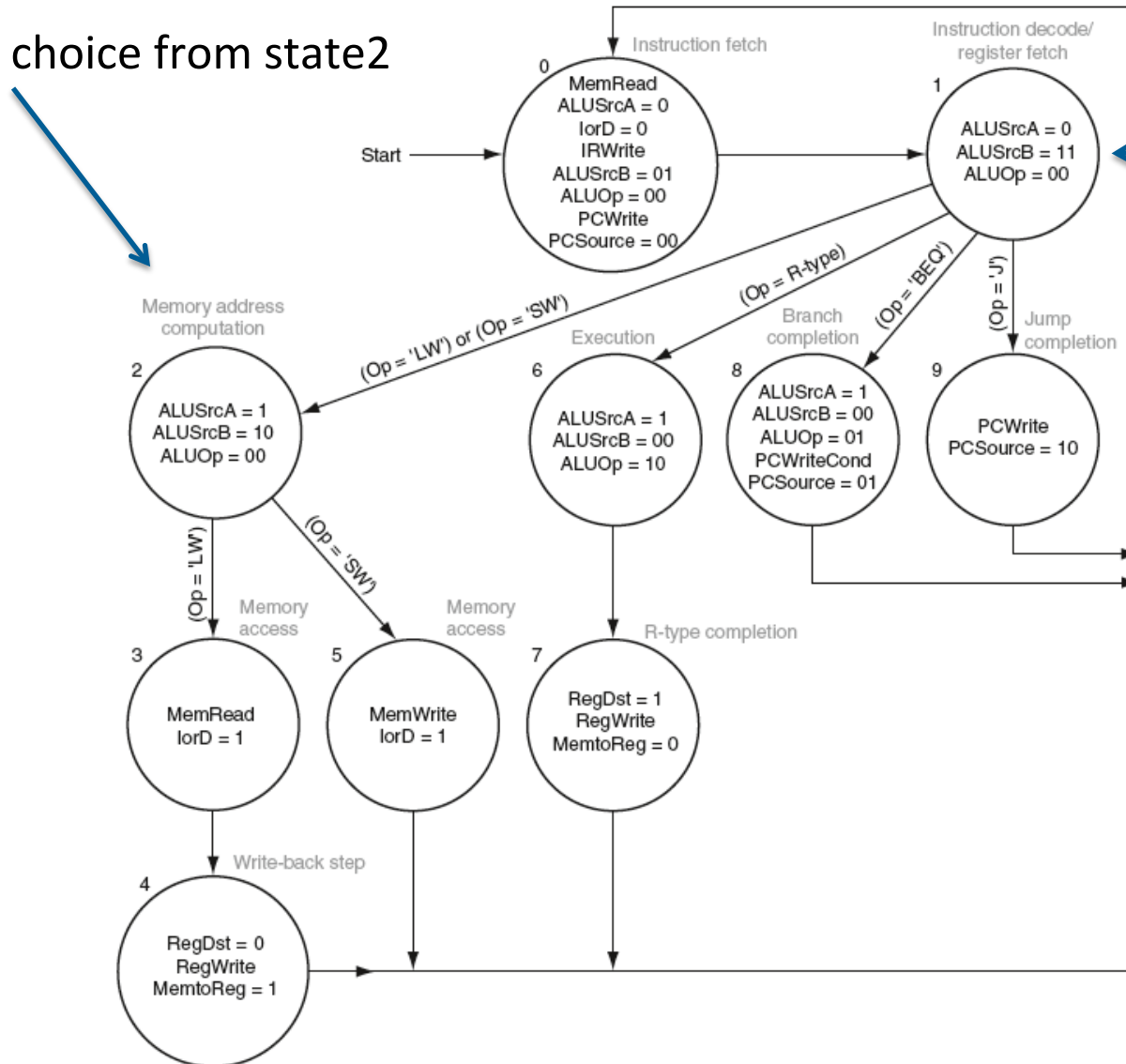4-way choice
from state1

To go to the next sequential state, just increment the current state


Set the state to 0 to go back to the initial state

Small lookup tables can be used to choose a non-sequential state

The choice from state 1 and from state2 is based on the opcode

Two ROMs (addressed by opcode) can be used

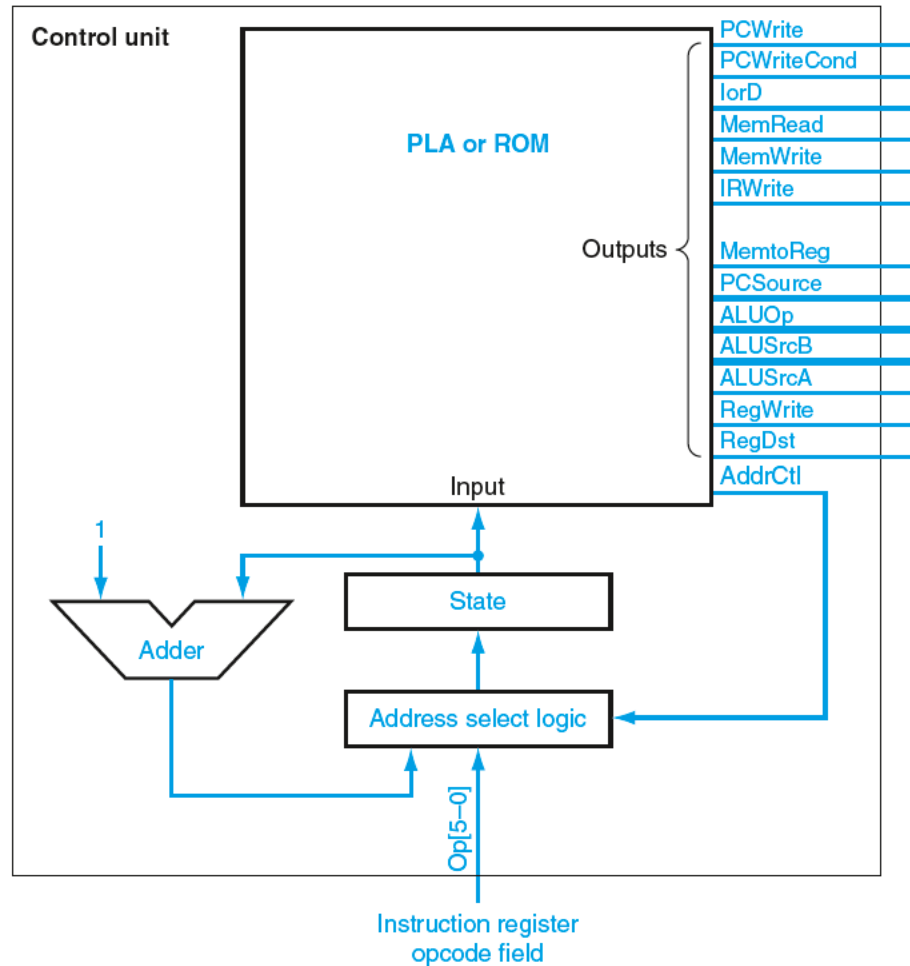A 2-bit control signal can be used with a MUX for 4 possible choices




2-bit AddrCtl causes Address select logic to output the next state number

AddrCtl is defined as follows:

AddrCtl value	Action
0	Set state to 0
1	Dispatch with ROM 1
2	Dispatch with ROM 2
3	Use the incremented state

In state1, next state is looked up in dispatch ROM1

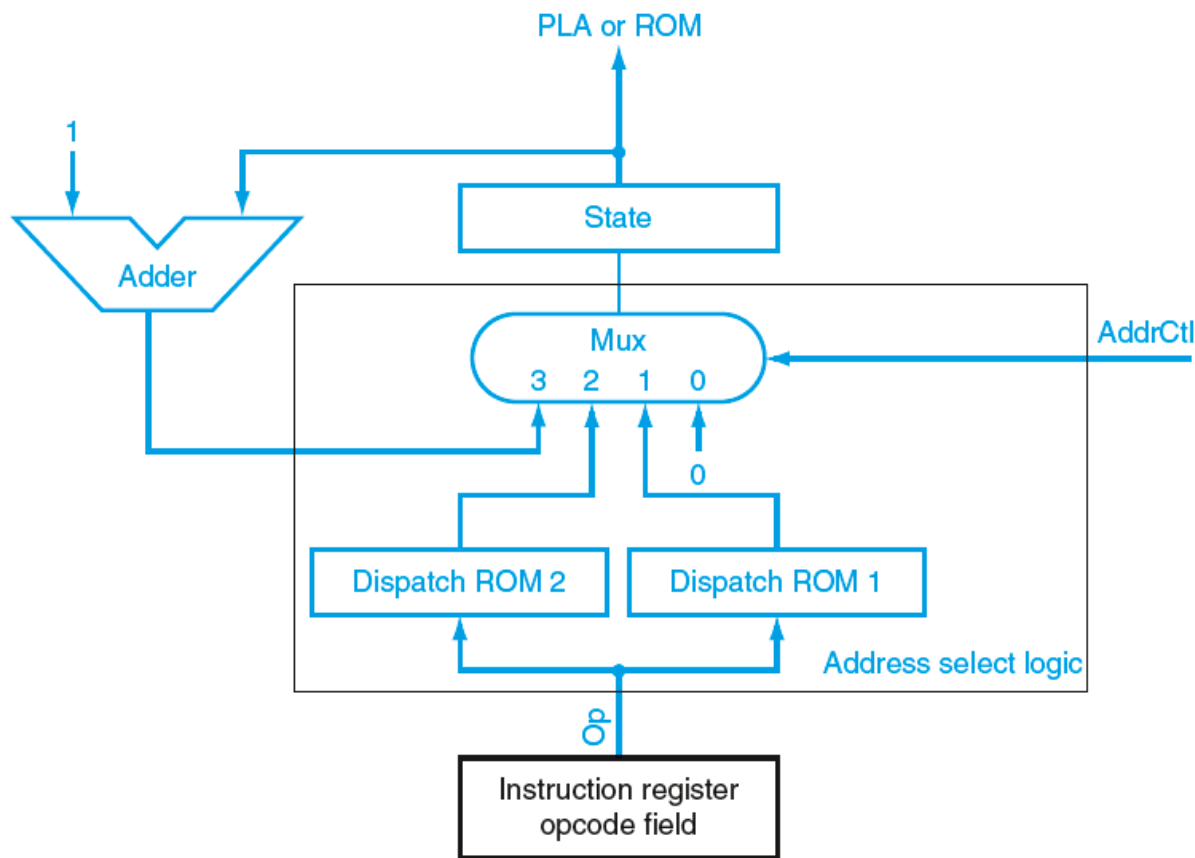In state2, next state is looked up in dispatch ROM2



AddrCtl selects from: 0, ROM1, ROM2 or Output of Adder as next state

Dispatch ROM 1		
Op	Opcode name	Value
000000	R-format	0110
000010	jmp	1001
000100	beq	1000
100011	lw	0010
101011	sw	0010

Dispatch ROM 2		
Op	Opcode name	Value
100011	lw	0011
101011	sw	0101

6-bit opcode as index implies up to $2^6 = 64$ entries
Only 5 entries are used from ROM1
Only 2 entries are used from ROM2

AddrCtl is determined just by the state number

State number	Address-control action	Value of AddrCtl
0	Use incremented state	3
1	Use dispatch ROM 1	1
2	Use dispatch ROM 2	2
3	Use incremented state	3
4	Replace state number by 0	0
5	Replace state number by 0	0
6	Use incremented state	3
7	Replace state number by 0	0
8	Replace state number by 0	0
9	Replace state number by 0	0

State number determines AddrCtl as well as datapath control bits

AddrCtl as well as datapath control bits can be stored in a control memory

State number	Control word bits 17–2	Control word bits 1–0
0	1001010000001000	11
1	0000000000011000	01
2	0000000000010100	10
3	0011000000000000	11
4	0000001000000010	00
5	0010100000000000	00
6	0000000001000100	11
7	0000000000000011	00
8	0100000010100100	00
9	1000000100000000	00


State number serves as address of all 18 bits (16 control + 2 AddrCtl)

Each 18-bit pattern can be viewed as a single “micro-instruction”

Micro-instructions are contained in the control store (ROM)

State number	Control word bits 17–2	Control word bits 1–0
0	1001010000001000	11
1	0000000000011000	01
2	0000000000010100	10
3	0011000000000000	11
4	0000001000000010	00
5	0010100000000000	00
6	0000000001000100	11
7	0000000000000011	00
8	0100000010100100	00
9	1000000100000000	00

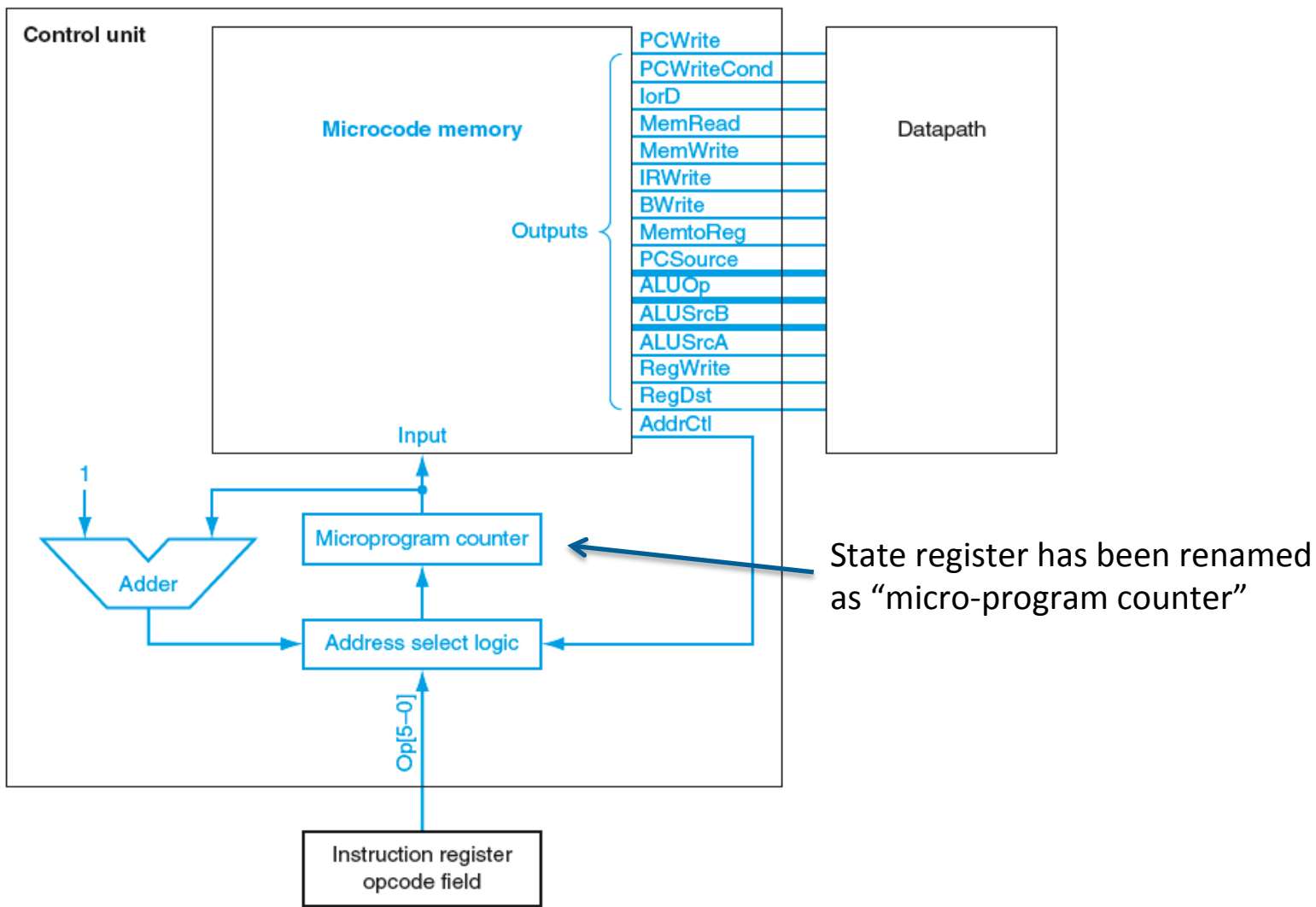Each micro-instruction takes one clock cycle



Field name	Value	Signals active	Comment
ALU control	Add	ALUOp = 00	Cause the ALU to add.
	Subt	ALUOp = 01	Cause the ALU to subtract; this implements the compare for branches.
	Func code	ALUOp = 10	Use the instruction's function code to determine ALU control.
SRC1	PC	ALUSrcA = 0	Use the PC as the first ALU input.
	A	ALUSrcA = 1	Register A is the first ALU input.
SRC2	B	ALUSrcB = 00	Register B is the second ALU input.
	4	ALUSrcB = 01	Use 4 as the second ALU input.
	Extend	ALUSrcB = 10	Use output of the sign extension unit as the second ALU input.
	Extshft	ALUSrcB = 11	Use the output of the shift-by-two unit as the second ALU input.
Register control	Read		Read two registers using the rs and rt fields of the IR as the register numbers and putting the data into registers A and B.
	Write ALU	RegWrite, RegDst = 1, MemtoReg = 0	Write a register using the rd field of the IR as the register number and the contents of ALUOut as the data.
	Write MDR	RegWrite, RegDst = 0, MemtoReg = 1	Write a register using the rt field of the IR as the register number and the contents of the MDR as the data.

Field name	Value	Signals active	Comment
Memory	Read PC	MemRead, lorD = 0, IRWrite	Read memory using the PC as address; write result into IR (and the MDR).
	Read ALU	MemRead, lorD = 1	Read memory using ALUOut as address; write result into MDR.
	Write ALU	MemWrite, lorD = 1	Write memory using the ALUOut as address, contents of B as the data.
PC write control	ALU	PCSource = 00, PCWrite	Write the output of the ALU into the PC.
	ALUOut-cond	PCSource = 01, PCWriteCond	If the Zero output of the ALU is active, write the PC with the contents of the register ALUOut.
	Jump address	PCSource = 10, PCWrite	Write the PC with the jump address from the instruction.
Sequencing	Seq	AddrCtl = 11	Choose the next microinstruction sequentially.
	Fetch	AddrCtl = 00	Go to the first microinstruction to begin a new instruction.
	Dispatch 1	AddrCtl = 01	Dispatch using the ROM 1.
	Dispatch 2	AddrCtl = 10	Dispatch using the ROM 2.

- Each micro-instruction performs one step in a machine instruction
- Each micro-instruction takes one clock cycle
- A machine instruction corresponds to a “micro-program”
- A micro-program is a sequence of micro-instructions
- Control memory containing micro-programs is on CPU chip
- Extra time is needed to retrieve and execute micro-programs


- Time required to retrieve micro-programs slows the system
- Micro-programming provides flexibility
- Complex instructions are easier to implement as micro-code
- CISC systems employ micro-programming
- Changing micro-code changes behavior of the system
- RISC systems use faster hardwired logic instead

- Each micro-instruction in our control ROM is 18 bits wide
- None of the fields within the micro-instructions are encoded
- This is fast since no decoding is required
- Systems of this type are said to be “minimally encoded”
- This is also called “horizontal micro-code”
- Micro-code is sometimes called firmware
- Firmware is harder to change than software
- Hardware is more difficult to change than firmware


- A writeable control store employs RAM for micro-code
- More realistic systems are more complex than our core MIPS
- Such systems could require very wide micro-instructions
- Encoding fields within these micro-instructions would save bits
- However these take longer to process due to need for decoding
- These systems employ maximally encoding (“vertical micro-code”)

- Micro-programming enables one system to behave like another
- This is called “emulation”
- It allows the same hardware to be used with different ISAs
- ISA is the instruction set architecture
- Different machine code can execute on the same hardware
- The micro-code is said to interpret the machine instructions

 Emulation allows the hardware to run different machine programs



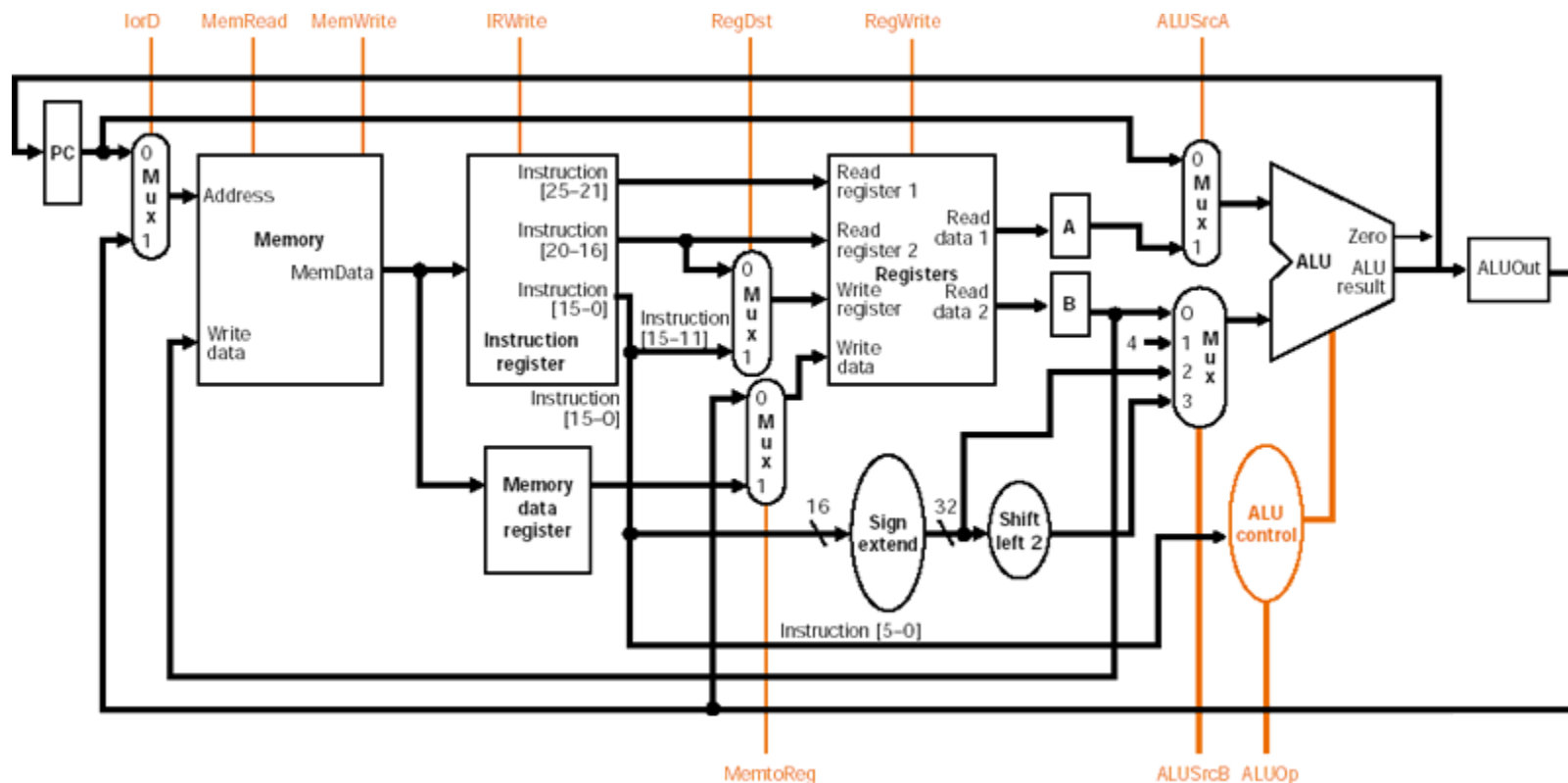
- Instructions can be executed in multiple steps
- Longest step determines clock period
 - Critical path: memory access time
 - Each step takes one clock cycle
- Different control signals are generated in different clock cycles
- Change in state occurs with each cycle
- Sequential logic contains state
- Finite-state machine can model behavior



- Component re-use eliminates duplication and reduces cost


Also called “state machine” or FSM and contains:

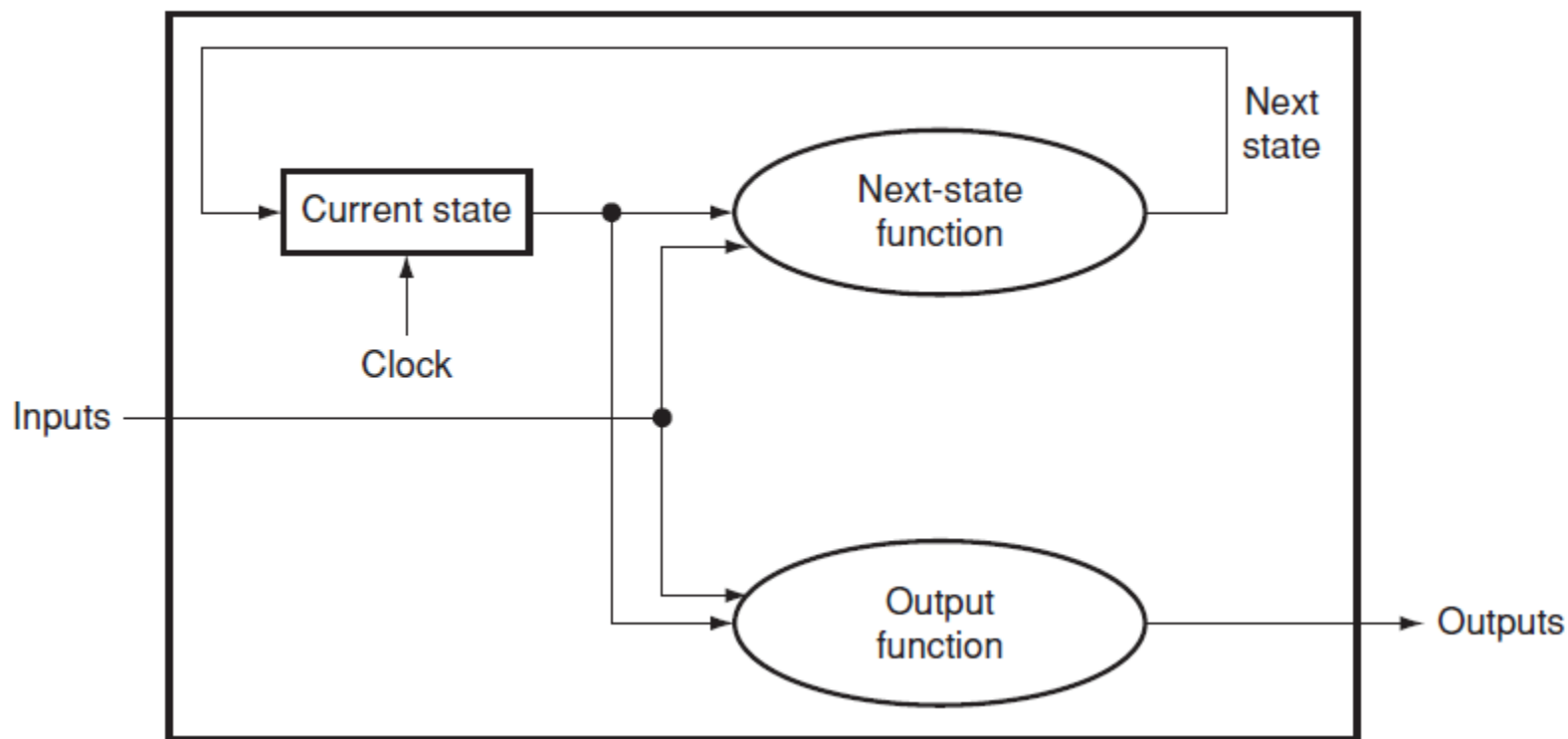- Set of states (one of which is the initial start state)
- Set of inputs
- Set of outputs
- Next-state function maps current state and inputs to a new state (state transition)
- Output function maps current state to set of outputs
 - Outputs may also depend on inputs
 - “Moore machine” outputs depend only on state
 - “Mealy machine” outputs depend on state and inputs



Sequential logic, internal storage contains the state information

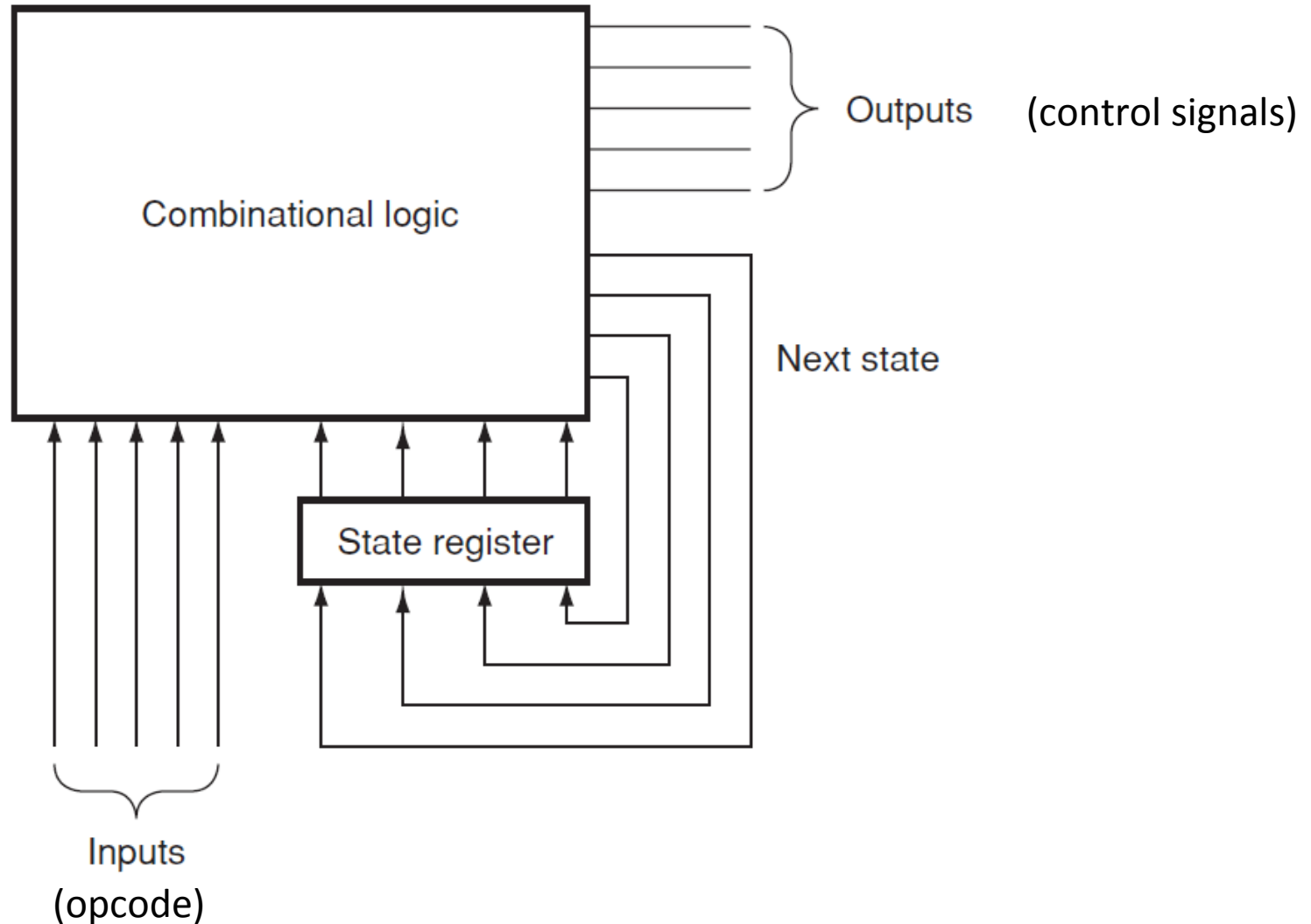- Set of inputs are the opcode bits
- Set of outputs are the control signals
- Next-state function is implemented with combinational logic
- New state is computed synchronously with clock cycle



MIPS core
instruction
subset requires
10 states

