

$A \oplus B$  and  $A \cdot B$  can be generated in parallel for each position

$S$  is then generated as  $A \oplus B \oplus C$  (where  $C$  is the carry-in)


Hence  $S_0$ , the LSB of the sum requires 2 gate delays

$C_{OUT}$  is available after 3 gate delays

Other sum bits need the carry from the bit position on the right

$S = A \oplus B \oplus C$ , so another gate delay is needed once  $C$  is available

 $C_{out} = (A \oplus B) \cdot C + A \cdot B$ , and requires 2 more gate delays



$S_0$  is available after 2 delays

$C_1$  is available after 3 delays

$S_1$  is available after  $1 + 3 = 4$  delays

$C_2$  is available after  $2 + 3 = 5$  delays

$S_2$  is available after  $1 + 5 = 6$  delays

$C_3$  is available after  $2 + 5 = 7$  delays

$S_3$  is available after  $1 + 7 = 8$  delays

$C_4$  is available after  $2 + 7 = 9$  delays

Recall that for the full adder:

$$\text{CarryOut} = (a \cdot b) + (a \oplus b) \cdot \text{CarryIn}$$

If  $a$  and  $b$  are both 1, they generate a CarryOut when added

If either  $a$  or  $b$  is 1, CarryIn is propagated to CarryOut

In general:  $c_{i+1} = (a_i \cdot b_i) + (a_i \oplus b_i) \cdot c_i = g_i + p_i \cdot c_i$

$g_i = a_i \cdot b_i$  and  $p_i = a_i \oplus b_i$  the subscript indicates the bit position

$C_0$  is the input carry for bit 0, the LSB

$C_0 = 0$  for addition


$C_0 = 1$  for subtraction

recurrence relation for all of the output carries:


$$c1 = g0 + p0 \cdot c0$$

$$c2 = g1 + p1 \cdot c1$$
 
$$c_i = g_{i-1} + p_{i-1} \cdot c_{i-1} \quad (\text{for } i > 0)$$



 
Inputs are the data bits for each position



Propagate & generate bits are used to produce carry bits

Carries require 2 gate delays and are produced in parallel

Lookahead carry generator circuit

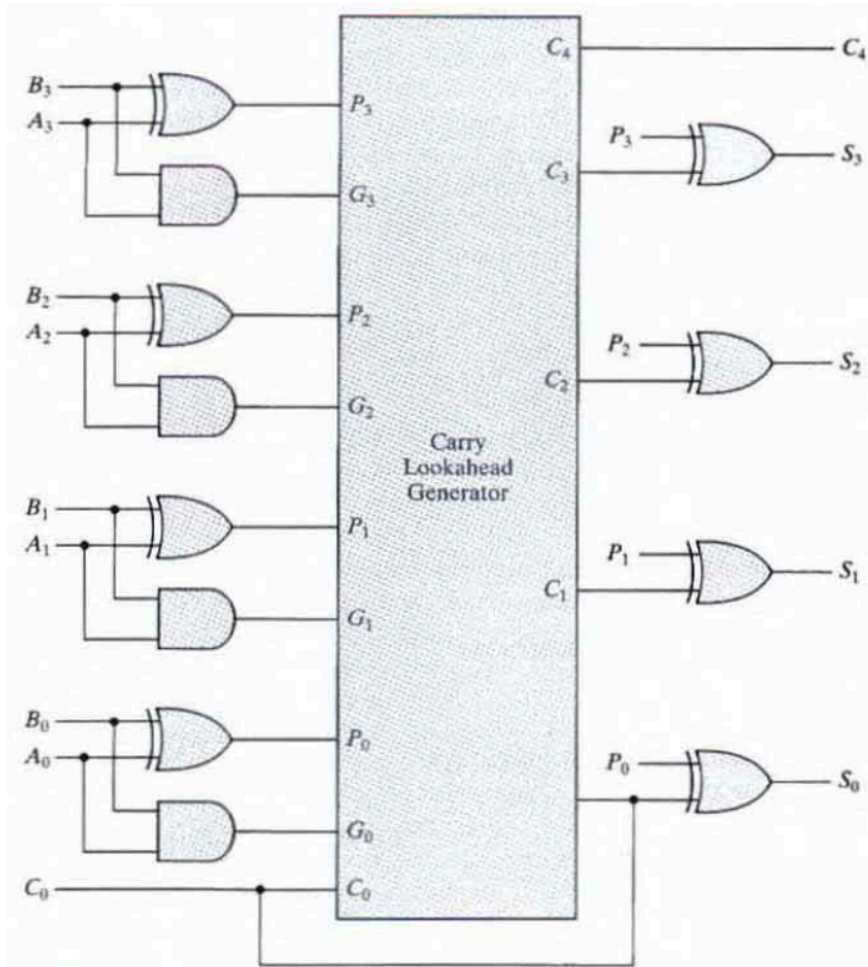

Bits in sum are available after  
 $1+2+1 = 4$  gate delays

4-bit adder with lookahead carry

- $c_0$  and all of the  $a_i$  and  $b_i$  bits are known up front
- All of the  $p_i$  and  $g_i$  can be generated in parallel (1 delay)
- All carry bits  $c_i$  are generated in parallel (2 more delays)
- All sum bits are produced in parallel (1 more delay)
- This is faster than the ripple carry adder
- Ripple carry adder computes each sum sequentially from LSB to MSB