 



- Combinational logic circuits need state elements to:
 - provide inputs
 - store the output
- State elements are sequential logic devices
 - Their output depends on the history of the inputs
- Combinational logic output depends only on current inputs



- State changes occur at clock edges



 A 1-bit memory device must capture and store its input



Cross coupled NOR gates


S and R are the inputs

The value of the output Q defines the state (0 or 1)

\overline{Q} (NOT Q) is the other output

Outputs do not change as long as S and R are both 0

 
In state 0, if S changes from 0 to 1, Q becomes 1



When S goes back to 0, Q retains its new value of 1



 In state 1, if R changes from 0 to 1, Q resets to 0



When R goes back to 0, Q retains its new value of 0

Behavior of the S-R Latch is described by a *characteristic table*
Defines output at $t+1$ (next cycle) as function of inputs at t

S	R	Q(t+1)
0	0	Q(t) no change
0	1	0
1	0	1
1	1	? unpredictable

Differs from truth table which shows output for current cycle



S-R Latch

Sets $Q = 1$ if S is asserted while clock is asserted

Sets $Q = 0$ if R is asserted while clock is asserted


S-R flip-flop

Sets $Q = 1$ if S is asserted at clock edge

Sets $Q = 0$ if R is asserted at clock edge

What is needed for single bit storage device is a D latch or flip-flop

 
D Latch has single data input and a clock input



The two AND gates open when C (clock) is high


Setting $D=1$ has same effect as $S=1$ and $R=0$ with S-R latch

 Setting $D=0$ has same effect as $R=1$ and $S=0$ with S-R latch



When *C*, the clock, is high, *Q* takes on the same value as *D*

D flip-flop (with falling edge trigger)

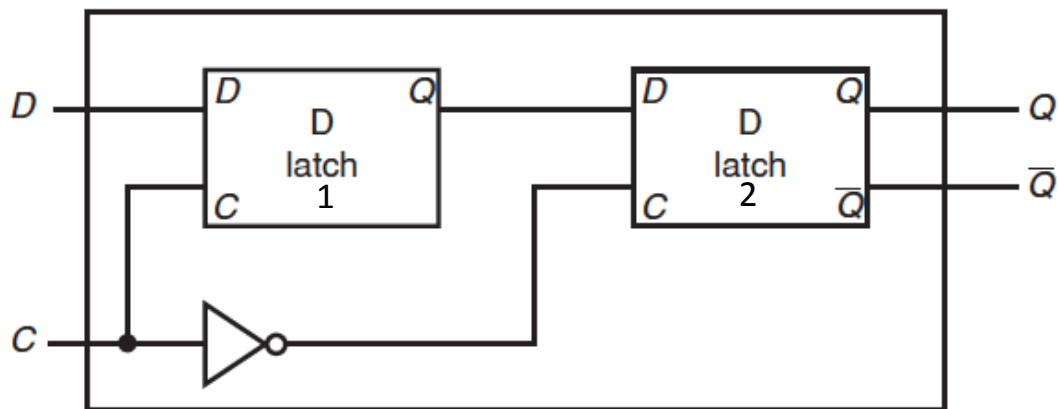


When C is high, latch 1 passes its input (D) to its output

When C goes low:

- output from latch 1 is retained
- Latch 2 passes output from latch 1 on to latch 2's output

 Q only changes when clock goes high and back low



Output Q changes at trailing clock edge in this example

The alternative would be leading edge trigger

As long as power is applied, the stored bit is retained