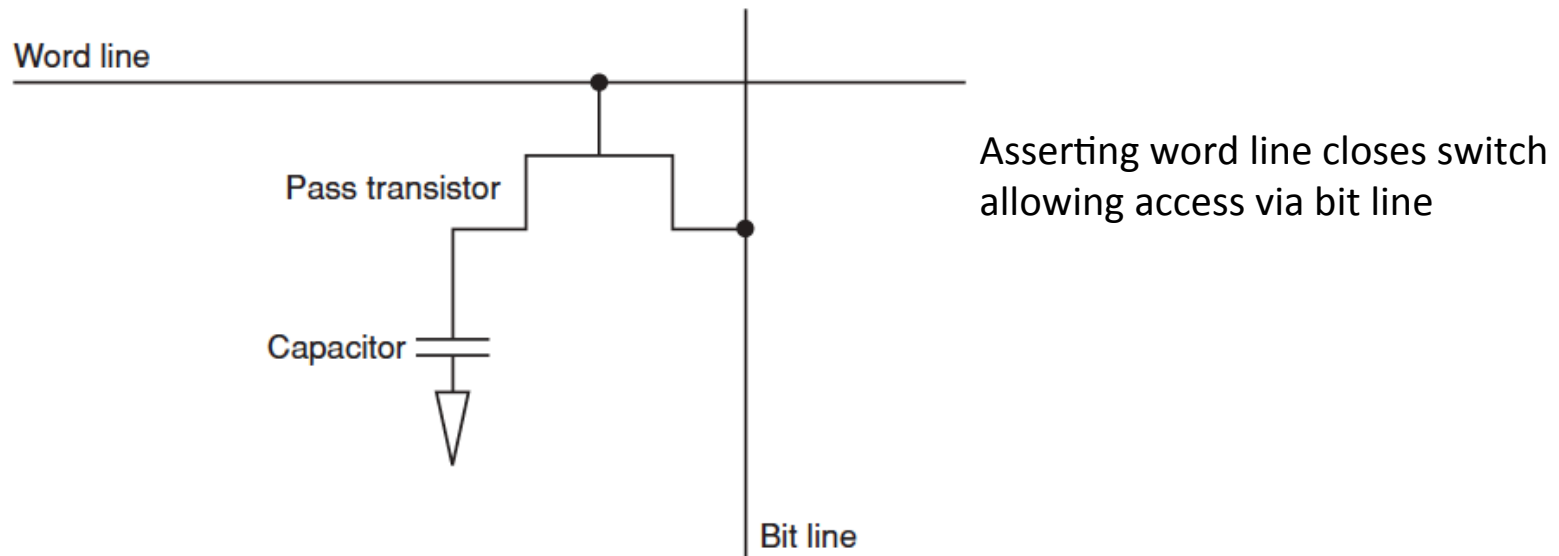


With dynamic RAM, the bit is stored as charge on a capacitor  
A transistor switch allows the bit to be read or written




Presence of charge represents 1

Absence of charge represents 0

Must refresh every few milliseconds to maintain the charge

Storage cells must have 2 stable states: 0 and 1 (*bi-stable*)

 
Another possible implementation uses cross-strapped inverters:



Stable output Q defines the state  
State does not change


$Q = 0$ :

 then  $\bar{Q} = 1$ ,  $Q = 0$  (consistent)



$Q = 1$ :

 
then  $\bar{Q} = 0$ ,  $Q = 1$  (consistent)



Stores 1 bit of state in the state variable,  $Q$  (or  $\bar{Q}$ )

No refresh is required

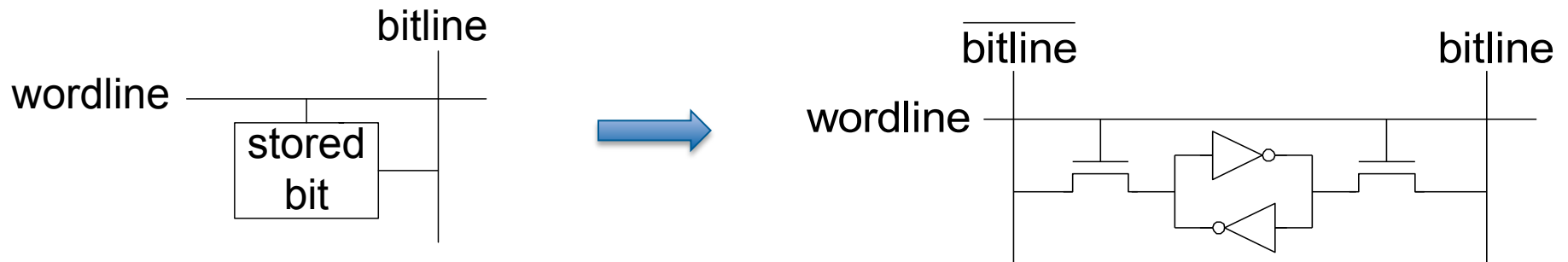Wordline and bitline allow access to the stored bit



Both switches turn on when wordline is asserted \_\_\_\_\_  
Stored bit can be transferred to or from bitline or bitline

Larger storage cells can be built using these single-bit devices

Flip-flops require more transistors to build

Cost, power and area consumed increases with more transistors

| Memory Type | Transistors per bit | Latency |
|-------------|---------------------|---------|
| Flip-flop   | 20 or more          | fast    |
| SRAM        | 6                   | medium  |
| DRAM        | 1                   | slow    |

Latency = time required to perform a read or write

Throughput = number of bits that can be accessed per unit time

Flip-flops have very short latencies and high throughput

SRAM has higher throughput and lower latency than DRAM

DRAM must wait for charge to move to bitline

DRAM must be refreshed periodically and after each read

In general, latency increases with larger memory sizes